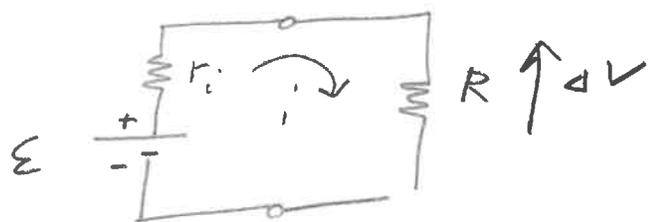


Chpt 28 Problems

①

①




$E = 12.6 \text{ V}$   
 $r_i = 0.056 \Omega$   
 $R = 4.60 \Omega$  (headlight)

$i = \frac{E}{r_i + R}$  since  $r_i + R = \text{total resistance}$

a)  $\Delta V = iR = E \left( \frac{R}{r_i + R} \right) = \boxed{12.4 \text{ volts}}$

b) If  $i = 35 \text{ A}$  is supplied by starter-motor, then  
 $\Delta V = iR = 35 \text{ A} \times 4.60 \Omega = \boxed{161 \text{ volts}}$

②

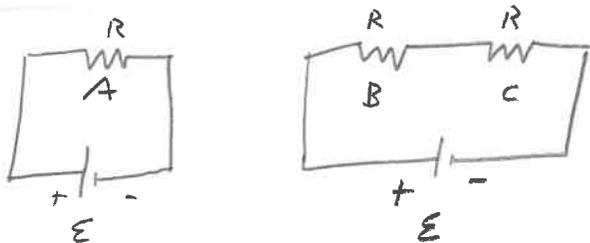

a)  $I_A = \boxed{\frac{E}{R}}$   
 $I_B = \boxed{\frac{E}{2R}}$ ,  $I_C = \boxed{\frac{E}{2R}}$

b) Brightness is proportional to power dissipated in each light bulb.

$P_A = I_A^2 R$

$P_B = I_B^2 R$

$P_C = I_C^2 R$



$P_B = P_C$  since  $I_B = I_C$


so same brightness  $\boxed{=}$

c) Note that  $I_B = I_C = \frac{1}{2} I_A$

Thus,  $P_B = \left( \frac{1}{2} I_A \right)^2 R = \frac{1}{4} I_A^2 R = \frac{1}{4} P_A$

so  $\boxed{P_A = 4P_B}$  (Brightness of A > Brightness of B) (or C)

3

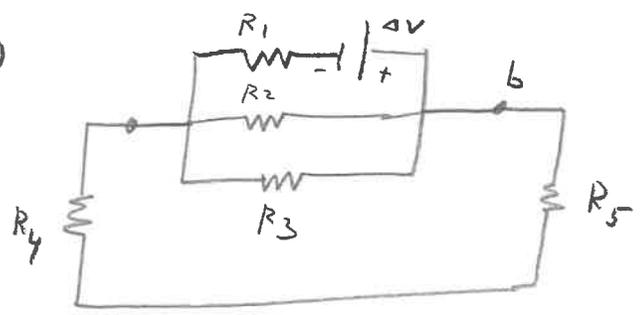

$\Delta V = 25 \text{ V}$   
 $R_1 = R_2 = 10 \Omega$   
 $R_3 = R_4 = 5 \Omega$   
 $R_5 = 18 \Omega$

2


a) Find current through  $R_5$

Combine  $R_4, R_5$  in series  $\rightarrow R_{45} = R_4 + R_5 = 23 \Omega$

Combine  $R_2, R_3, R_{45}$  in //  $\rightarrow R_{11} = \frac{1}{\frac{1}{R_2} + \frac{1}{R_3} + \frac{1}{R_{45}}}$

$$= \frac{1}{\frac{1}{10} + \frac{1}{5} + \frac{1}{23}}$$

$$= 2.91 \Omega$$

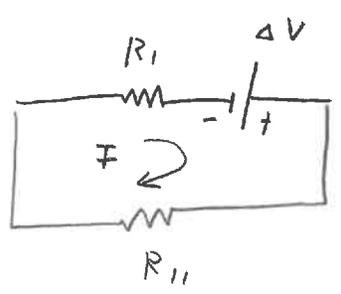


$$I = \frac{\Delta V}{R_1 + R_{11}} = \frac{25 \text{ volt}}{10 \Omega + 2.91 \Omega}$$

$$\Delta V_{11} = I R_{11} = 5.64 \text{ volts}$$


$$I_5 = \frac{\Delta V_{11}}{R_{45}} = \frac{5.64 \text{ volt}}{23 \Omega} = \boxed{0.245 \text{ amp}}$$

b)  $\Delta V_{ab} = \Delta V_{11} = \boxed{5.64 \text{ volt}}$


4.

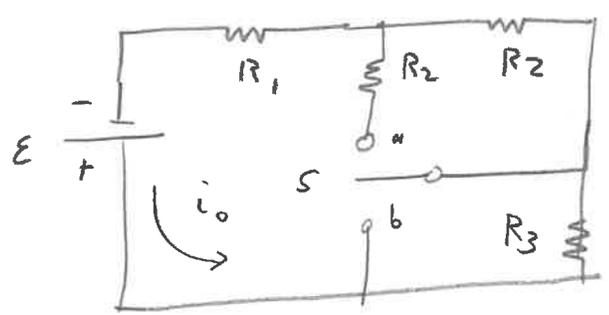

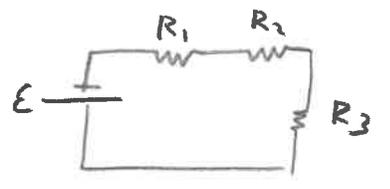$\mathcal{E} = 3 \text{ V}$   
 Switch open:  
 $i_0 = \frac{\mathcal{E}}{R_1 + R_2 + R_3} = 1.09 \text{ mA}$






Position a:

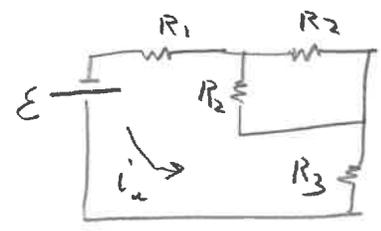

$$i_a = \frac{\mathcal{E}}{R_1 + \frac{R_2}{2} + R_3} = 1.22 \text{ mA}$$

Position b:

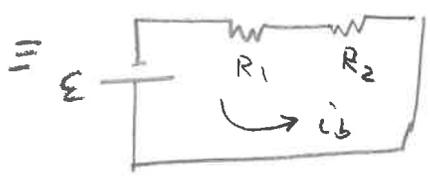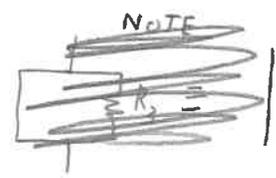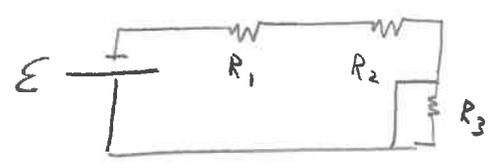

$$i_b = \frac{\epsilon}{R_1 + R_2} = 2.01 \text{ mA}$$

Thus,  $R_1 + R_2 + R_3 = \frac{\epsilon}{i_0} \equiv C_1 = 2752 \Omega$  (1)

$$R_1 + \frac{R_2}{2} + R_3 = \frac{\epsilon}{i_a} \equiv C_2 = 2459 \Omega$$
 (2)


$$R_1 + R_2 = \frac{\epsilon}{i_b} \equiv C_3 = 1493 \Omega$$
 (3)

(c) Subtract (3) from (1)  $\rightarrow R_3 = C_1 - C_3 = 1,26 \text{ k}\Omega$

(b) Subtract (2) from (1)  $\rightarrow \frac{R_2}{2} = C_1 - C_2 \rightarrow R_2 = 2(C_1 - C_2) = 0,587 \text{ k}\Omega$

(a) Then  $R_1 = C_3 - R_2 = 0,906 \text{ k}\Omega$

(5)

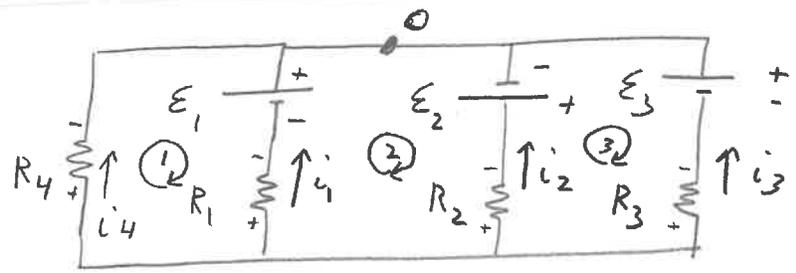

- $E_1 = 40 \text{ V}$
- $E_2 = 360 \text{ V}$
- $E_3 = 80 \text{ V}$
- $R_1 = 80 \Omega$
- $R_2 = 20 \Omega$
- $R_3 = 70 \Omega$
- $R_4 = 200 \Omega$

(a) Junction rule at o:  $i_1 + i_4 = i_2 + i_3$  (1)

Loop rule 1:  $-i_4 R_4 - E_1 + i_1 R_1 = 0$  (2)

Loop rule 2:  $-i_1 R_1 + E_1 + E_2 + i_2 R_2 = 0$  (3)

Loop rule 3:  $-i_2 R_2 - E_2 - E_3 + i_3 R_3 = 0$  (4)

Convert above 4 equations into a matrix equations.

Matrix Equations

$$\begin{bmatrix} 1 & -1 & -1 & 1 \\ R_1 & 0 & 0 & -R_4 \\ -R_1 & R_2 & 0 & 0 \\ 0 & -R_2 & R_3 & 0 \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \\ i_3 \\ i_4 \end{bmatrix} = \begin{bmatrix} 0 \\ E_1 \\ -E_1 - E_2 \\ E_2 + E_3 \end{bmatrix}$$

Solving matrix equation

$$M \vec{v} = \vec{w}$$


$$\rightarrow \vec{v} = M^{-1} \vec{w} \quad \text{when } M^{-1} \text{ is inverse matrix of } M$$

substituting the values for  $\mathcal{E}_1, \mathcal{E}_2, \mathcal{E}_3$  and  $R_1, R_2, R_3, R_4$

$$\rightarrow \begin{array}{l} i_1 = 5.14 \text{ amp} \quad (80 \Omega) \\ i_2 = 0.55 \text{ amp} \quad (20 \Omega) \\ i_3 = 6.42 \text{ amp} \quad (70 \Omega) \\ i_4 = 1.85 \text{ amp} \quad (200 \Omega) \end{array}$$

$$\begin{aligned} (6) \quad \Delta V_3 &= -R_3 i_3 \\ &= -70 \Omega \times 6.42 \text{ Amp} \\ &= \boxed{-451 \text{ volt}} \end{aligned}$$

(6.)

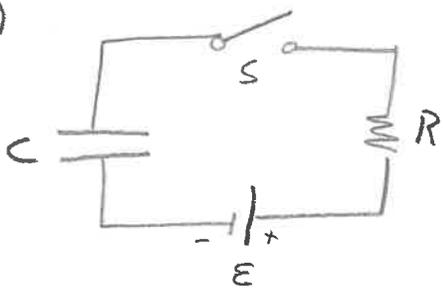


$$\begin{aligned} R &= 3 \text{ M}\Omega = 3 \times 10^6 \Omega \\ C &= 6 \mu\text{F} = 6 \times 10^{-6} \text{ F} \\ \mathcal{E} &= 34 \text{ V} \end{aligned}$$

(charging capacitor)

$$a) \quad \tau = RC = \boxed{18 \text{ s}}$$

$$b) \quad \Delta V_{\max} = \mathcal{E} \rightarrow Q_{\max} = C \Delta V_{\max} = C \mathcal{E} = \boxed{204 \mu\text{C}}$$
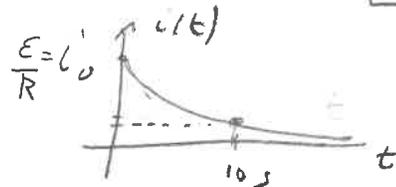
$$\begin{aligned} c) \quad i(t) &= i_0 e^{-t/RC} \\ &= \frac{\mathcal{E}}{R} e^{-t/RC} \end{aligned}$$




$$i(t=10 \text{ s}) = \frac{34 \text{ V}}{3 \times 10^6 \Omega} e^{-10 \text{ s} / 18 \text{ s}}$$

$$= \boxed{6.5 \text{ mA}}$$

7.) Heater :  $P_1 = 2 \times 10^3 \text{ W}$   
 Toaster :  $P_2 = 500 \text{ W}$   
 Grill :  $P_3 = 1000 \text{ W}$   
 $\Delta V = 120 \text{ V}$


- a)  $I_1 = P_1 / \Delta V = 16.67 \text{ amp}$   
 $I_2 = P_2 / \Delta V = 4.167 \text{ amp}$   
 $I_3 = P_3 / \Delta V = 8.33 \text{ amp}$
- b)  $I_{\text{tot}} = I_1 + I_2 + I_3 = 29.16 \text{ amp} < 30 \text{ amp}$   
 So circuit breaker will not be tripped

8.)

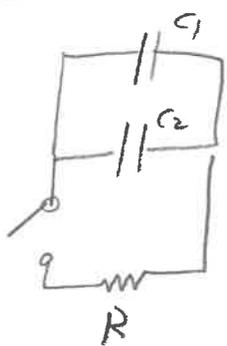

$C_1 = 3 \mu\text{F}$   
 $C_2 = 2 \mu\text{F}$   
 $R = 500 \Omega$   
 $\Delta V = 24 \text{ volts}$   
 (discharging capacitor)

Equivalent circuit

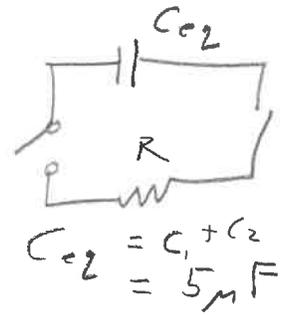

$Q_{eq} = C_{eq} \Delta V = 120 \mu\text{C}$   
 (total initial charge on  $C_1$  and  $C_2$ )

When discharging:


$q_{eq}(t) = Q_{eq} e^{-t/\tau}$  where  $\tau = RC_{eq} = 2.5 \text{ ms}$

when  $t = 3 \text{ ms}$ ,  $q_{eq}(t=3 \text{ ms}) = 61.44 \mu\text{C}$

$\Delta V(t=3 \text{ ms}) = \frac{q_{eq}(t=3 \text{ ms})}{C_{eq}} = 12.3 \text{ volts}$

- a) Thus,  $Q_1(t=3 \text{ ms}) = C_1 \Delta V(t=3 \text{ ms}) = 36.9 \mu\text{C}$   
 b)  $Q_2(t=3 \text{ ms}) = C_2 \Delta V(t=3 \text{ ms}) = 24.6 \mu\text{C}$   
 c)  $i(t=3 \text{ ms}) = \frac{\Delta V(t=3 \text{ ms})}{R} = 24.6 \text{ mA}$

9.

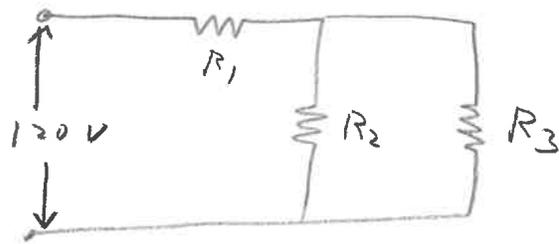

$$R_1 = R_2 = R_3 = R$$


$$P = 45 \text{ W}$$

$$\Delta V = 120 \text{ V}$$

Recall:  $P = \frac{(\Delta V)^2}{R} \Rightarrow R = \frac{(\Delta V)^2}{P} = \frac{(120 \text{ V})^2}{45 \text{ W}} = 320 \Omega$

6

a) Equivalent circuit

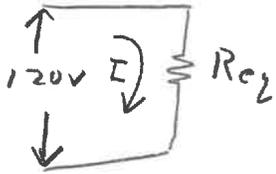

Where  $R_{eq} = R_1 + R_{23}$   
 $R_{23} = \frac{1}{\frac{1}{R_2} + \frac{1}{R_3}} = \frac{1}{\frac{1}{R} + \frac{1}{R}} = \frac{R}{2}$

$$\rightarrow R_{eq} = R + \frac{R}{2} = \frac{3R}{2}$$

Total power supplied by source:

$$P_{tot} = \Delta V \cdot I = \Delta V \cdot \left( \frac{\Delta V}{R_{eq}} \right) = \frac{(\Delta V)^2}{\frac{3R}{2}} = \frac{2}{3} P = \boxed{30 \text{ watts}}$$

(Equivalently,  $I = \left( \frac{\Delta V}{R_{eq}} \right) = \frac{\Delta V}{\left( \frac{3R}{2} \right)} = \frac{2}{3} \left( \frac{\Delta V}{R} \right) = 0.25 \text{ A}$ )

$$\rightarrow P_{tot} = \Delta V \cdot I = 120 \text{ V} (0.25 \text{ A}) = 30 \text{ watts}$$

b)  $\Delta V_1 = R_1 \cdot I = R \cdot I = \boxed{80 \text{ volts}}$   
 $\Delta V_2 = \Delta V_3 = R_{23} \cdot I = \frac{R}{2} \cdot I = \boxed{40 \text{ volts}}$